

ELEC 457

Assignment-5


Sait Berk VARIMLI

141024054

I prepared this homework in 7 hours.

 Problem 1


Implement the following logic circuit **as is** in your synthesis tool.




Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity invertand is
Port (
a : in std_logic;
b : in std_logic;
x : out std_logic );
end invertand;
architecture Behavioral of invertand is
signal b1,b2,b3 : std_logic;
begin
b1 <= not b;
b2 <= not b1;
b3 <= not b2;
x <= a and b3;
end Behavioral;
```

Elaborated Schematic:

 

Implementation Schematic:

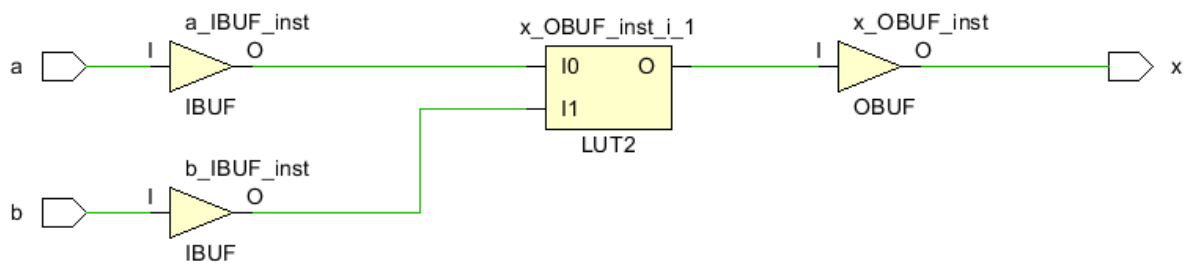

Report Utilization:

Name	Slice LUTs (53200)	Slice (13300)	LUT as Logic (53200)	Bonded IPADs (2)
N invertand	1	1	1	3

Problem 2

Design and simulate a **shift register**. You should have a generic that defines how many flip-flop stages your input should be delayed.

Code:

```

library ieee;
use ieee.std_logic_1164.all;
entity shiftr is
  generic(
    N : integer := 32
  );
  port(
    clk : in std_logic;
    input : in std_logic;
    output : out std_logic
  );
end entity shiftr;
  
```

```

    );
end shiftr;

architecture rtl_a of shiftr is
    signal s_i : std_logic_vector(N - 1 downto 0);
begin
    process(clk) is
    begin
        if rising_edge(clk) then
            s_i <= s_i(N - 2 downto 0) & input;
        end if;
    end process;

    output <= s_i(N);

end rtl_a;

architecture rtl_b of shiftr is
    signal s_i : std_logic_vector(N - 1 downto 0);
begin
    process(clk) is
    begin
        if rising_edge(clk) then
            for i in 0 to N - 2 loop
                s_i(i+1) <= s_i(i);
            end loop;
            s_i(0) <= input;
        end if;
    end process;

    output <= s_i(N - 1);

end rtl_b;

```

Testbench code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tb_shiftr is
end tb_shiftr;
architecture Behavioral of tb_shiftr is
    component shiftr is
        generic(
            N : integer := 32
        );
        port(
            clk : in std_logic;
            input : in std_logic;
            output : out std_logic
        );
    end component;
    signal clk,input,output : std_logic;
    begin
        h0: shiftr port map(
            clk=>clk, input=>input, output=>output);
        process
        begin
            wait for 50ns;
            clk <= '0';
            input <= '0';
            wait for 10ns;
            clk <= '1';
            input <= '1';
            wait for 10ns;
            clk <= '0';
            input <= '1';
            wait for 10ns;
```

```

clk <= '1';
input <= '0';
wait for 10ns;
clk <= '0';
input <= '1';
wait for 10ns;
clk <= '1';
input <= '0';
wait;
end process;
end Behavioral;


```

Simulation:


I got problem in simulation, i couldn't fix it.

		1,0	
Name	Value	999,998 ps	999,999 ps
clk	1		
input	0		
output	U		

Elaborated Schematic:

 

Implementation Schematic:

 

Report Utilization:

Name	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Memory (17400)	Block RAM Tile (140)	Bonded IPADs (2)	BUFIO (16)
N shiftr	1	2	2	1	2	3	1

Problem 4

Design and simulate a 32-bit count-down timer.

- Timer should count down from the given M value, and whenever it reaches to 0, it should generate a done flag.
- Timer should be free-running meaning it should keep running as long as the enable port is held high.
- Timer should generate the done flag when the Mth value is reached. M is given as generic.

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity counter is
generic ( M: integer := 2**20);
Port (
clk, rst, i_en : in std_logic;
o_tick_s, o_tick_v : out std_logic
);
end counter;

architecture rtl of counter is
    signal led_int : std_logic := '0';
    signal tick : std_logic := '0';
    signal s_cnt, v_cnt : unsigned(31 downto 0);
begin
    process (clk) is
    begin
        if rising_edge(clk) then
            if rst = '1' then
                s_cnt <= to_unsigned(M-1, 32);
            elsif i_en = '1' then
```



```

if s_cnt=0 then
s_cnt <= to_unsigned(M,32);
else
s_cnt <= s_cnt -1;
end if;
end if;
end if;
end process;
process(clk) is
begin
if rising_edge(clk) then
if rst = '1' then
v_cnt <= to_unsigned(M-1,32);
elsif i_en ='1' then
if v_cnt=0 then
v_cnt<=to_unsigned(M,32);
else
v_cnt<=v_cnt-1;
end if;
end if;
end if;
end process;

o_tick_s <= '1' when s_cnt = 0 else '0';
o_tick_v <= '1' when v_cnt = 0 else '0';

end rtl;

```

Testbench code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```
entity tb_counter is
end tb_counter;
```

```
architecture Behavioral of tb_counter is
```

```
component counter is
generic(M: integer := 20);
port( clk, rst, i_en : in std_logic;
o_tick_s, o_tick_v : out std_logic);
end component;
```

```
signal clk,rst,i_en,o_tick_s,o_tick_v : std_logic;
```

```
begin
h0: counter port map(
clk=>clk, rst=>rst, i_en=>i_en, o_tick_s=>o_tick_s, o_tick_v=>o_tick_v);
process
begin
wait for 10ns;
clk <= '1';
rst <= '1';
i_en <= '0';
wait for 5 ns;
clk <= '1';
i_en <= '0';
rst <= '0';
wait for 5 ns;
clk <= '0';
i_en <= '1';
rst <= '0';
wait for 5 ns;
clk <= '1';
i_en <= '0';
```

```

rst <= '0';
wait for 5 ns;
end process;

```


```

end Behavioral;


```

Simulation:

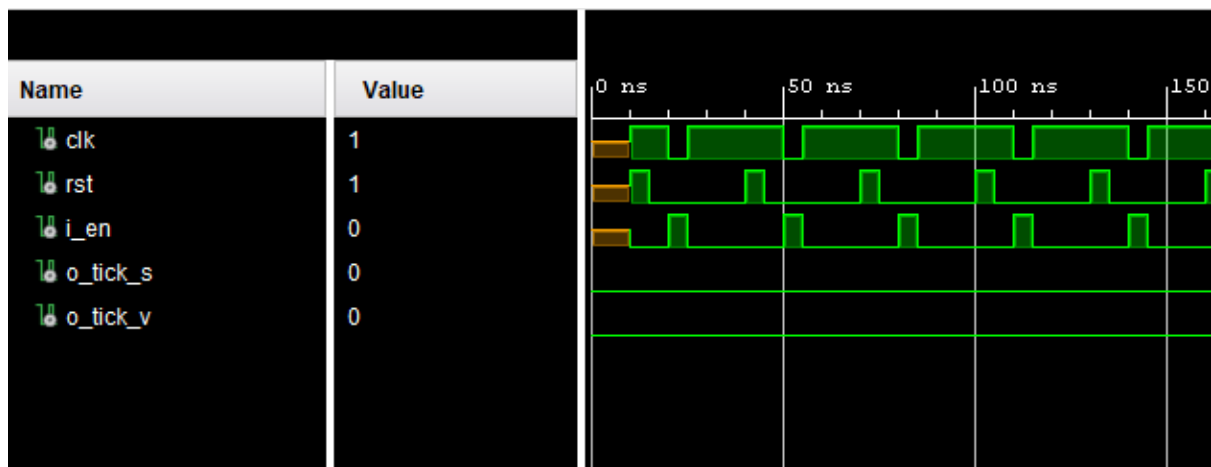
I had to leave from last lecture's lab so i couldn't prepare working simulation.



Elaborated Schematic:

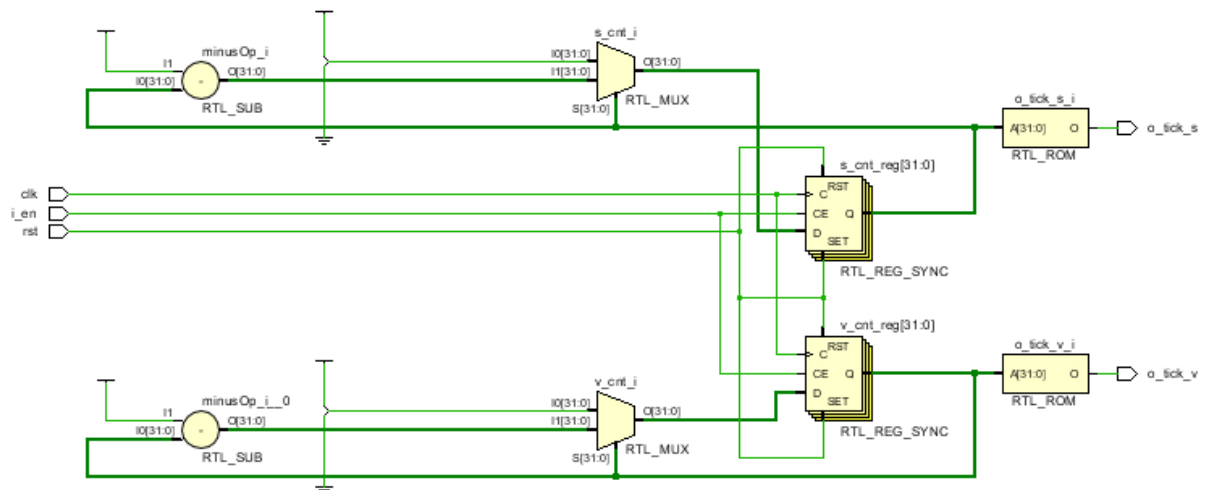

Implementation Schematic:

 

Report Utizilation:

Name ^1	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Logic (53200)	Block RAM Tile (140)	Bonded IPADs (2)	BUFIO (16)
N counter	140	64	43	140	64	5	1

Problem 5

Design and simulate a 6-bit up / down counter.

- There should be an input to choose between up and down modes.
- The counter value should be the output.
- Use your circuit from problem 1 for slowing down your counter for human interaction (you can choose a big M to slow down).
- Simulate & verify circuit operation.
- You may implement this on the boards. Choose RGB Leds as outputs, a switch to enable, and another switch to choose the direction of the counter.

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity up_down_6_bit is
Port(clock : in std_logic;
u : in std_logic;
d : in std_logic;
pren : in std_logic;
q : out std_logic_vector(5 downto 0));
end up_down_6_bit;
architecture Behavioral of up_down_6_bit is
signal reg: std_logic_vector (5 downto 0);
begin
process(pren, clock)
begin
if(pren='0') then
reg<="111111";
elsif(clock'event and clock='1') then
if(u='1' and d='0') then
reg<=reg + '1';
elsif(u='0' and d='1') then
reg<=reg-'1';
```

```

else
reg<=reg;
end if;
end if;
end process;
q <= reg;
end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tb_updown6bit is
-- Port ( );
end tb_updown6bit;

```

```

architecture Behavioral of tb_updown6bit is
component up_down_6_bit
port(
clock : in std_logic;
u : in std_logic;
d : in std_logic;
pren : in std_logic;
q : out std_logic_vector(5 downto 0));
end component;

```

```

signal clock,u,d,pren : std_logic :='0';
signal q : std_logic_vector(5 downto 0);
constant clock_period : time := 10ns;
begin
u0: up_down_6_bit port map(
clock=>clock, u=>u, d=>d, pren=>pren, q=>q);
clock_process : process

```

```

begin
clock <= '0';
wait for clock_period/2;
clock <='1';
wait for clock_period/2;
end process;
stim_proc: process
begin
pren <= '0';
wait for 40ns;
pren <='1';
u<='1';
d<='0';
wait for 40 ns;
pren<='1';
u<='1';
d<='0';
wait for 40 ns;
pren<='1';
u<='0';
d<='1';
wait for 40 ns;
pren<='1';
u<='1';
d<='1';
wait for 40 ns;
pren<='1';
u<='0';
d<='0';
wait for 40 ns;
pren <='1';
u<='0';

```


```

d<='0';
wait;
end process;


end Behavioral;

```


Simulation:

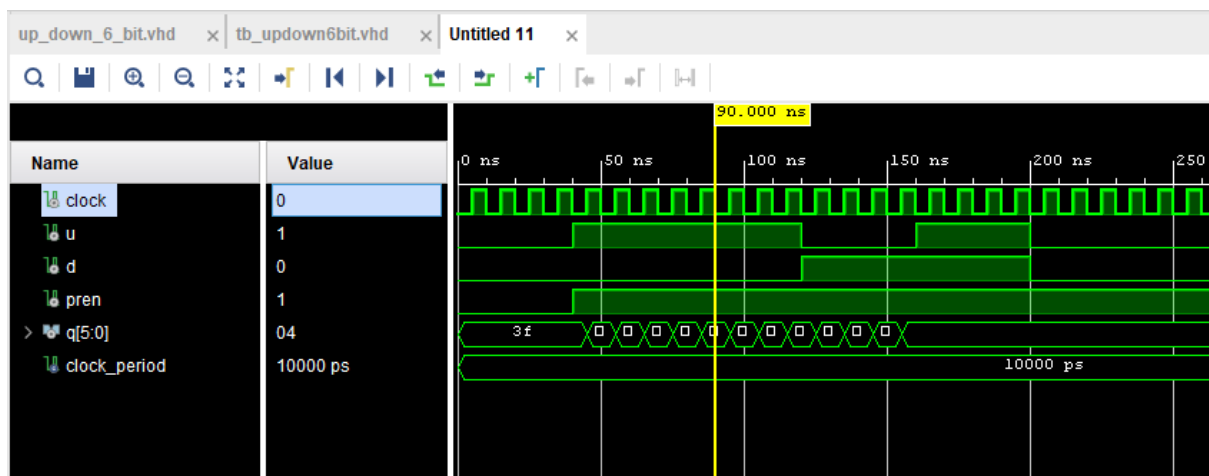

Elaborated Schematic:

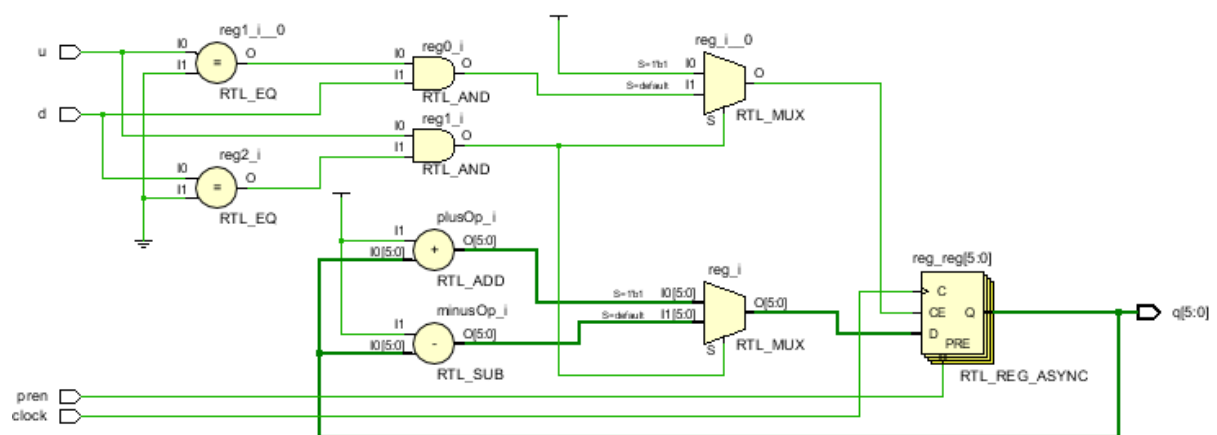

Implementation Schematic:

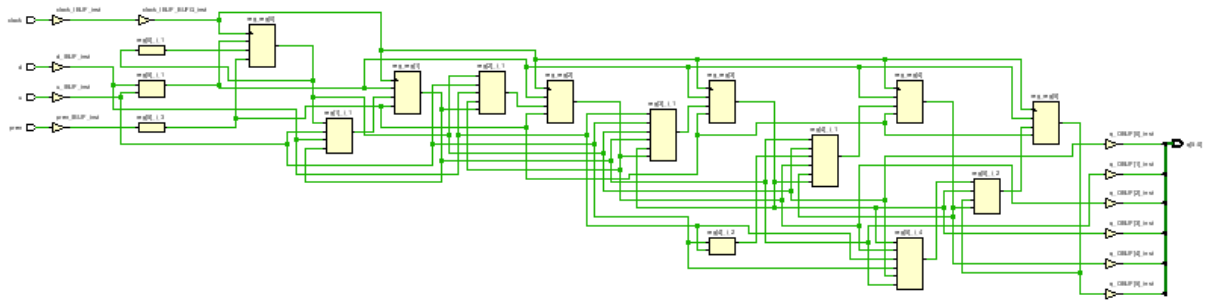

Report Utilization:

Name	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Logic (53200)	Block RAM Tile (140)	Bonded IPADs (2)	BUFIO (16)
up_down_6_bit	8	6	2	8	6	10	1