

ELEC 457

ASSIGNMENT-6

Sait Berk VARIMLI


141024054

This assignment took 7.5 hours for finish.

(First question 30min. , second question 2 hours, third question 5 hours)

Problem 1

Design the state machine given below.

 

Code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;entity state is
port(
    clk, rst : in std_logic;

    a : in std_logic_vector(1 downto 0); -- a[0] for A a[1] for B

    moore : out std_logic
);
end state;

architecture Behavioral of state is
type state_type is (s0, s1, s2);
signal state, state_next : state_type := s0;
begin
    process(clk) is
    begin
        if rising_edge(clk) then
```

```

    if rst = '1' then

        state <= s0;

    else

        state <= state_next;

    end if;

end if;

end process;

process(state, a) is
begin

    case state is

        when s0 =>

            if a = "10" then

                state_next <= s1;

            elsif a = "10" then

                state_next <= s2;

            else

                state_next <= s0;

            end if;

        when s1 =>

            if a = "01" then

                state_next <= s2;

            elsif a = "10" then

                state_next <= s0;

            else

                state_next <= s1;

            end if;

        when s2 =>

```

```

        state_next <= s0;

    end case;

end process;

process(state) is
begin
    case state is
        when s0 | s1 =>
            moore <= '0';

        when s2 =>
            moore <= '1';

    end case;

end process;

end Behavioral;

```

Testbench Code:

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity tb_state is
end tb_state;

architecture Behavioral of tb_state is

    component state is

        port(

            clk, rst : in std_logic;

            a : in std_logic_vector(1 downto 0);

            moore : out std_logic

        );

    end component;

```

```

signal clk,rst,moore : std_logic;

signal a : std_logic_vector(1 downto 0);

begin


h0 : state port map(

clk => clk, rst => rst, a=>a, moore=>moore);

clock_process :process

begin

rst <='0';

clk <='0';

wait for 5 ns;

clk <= '1';

wait for 5 ns;

end process;


process

begin

wait for 50 ns;

a <= "10";

wait for 10 ns;

a <= "01";

wait for 10 ns;

a <= "10";

wait for 10 ns;

a <= "00";


wait;

end process;


end Behavioral;

```


Simulation:

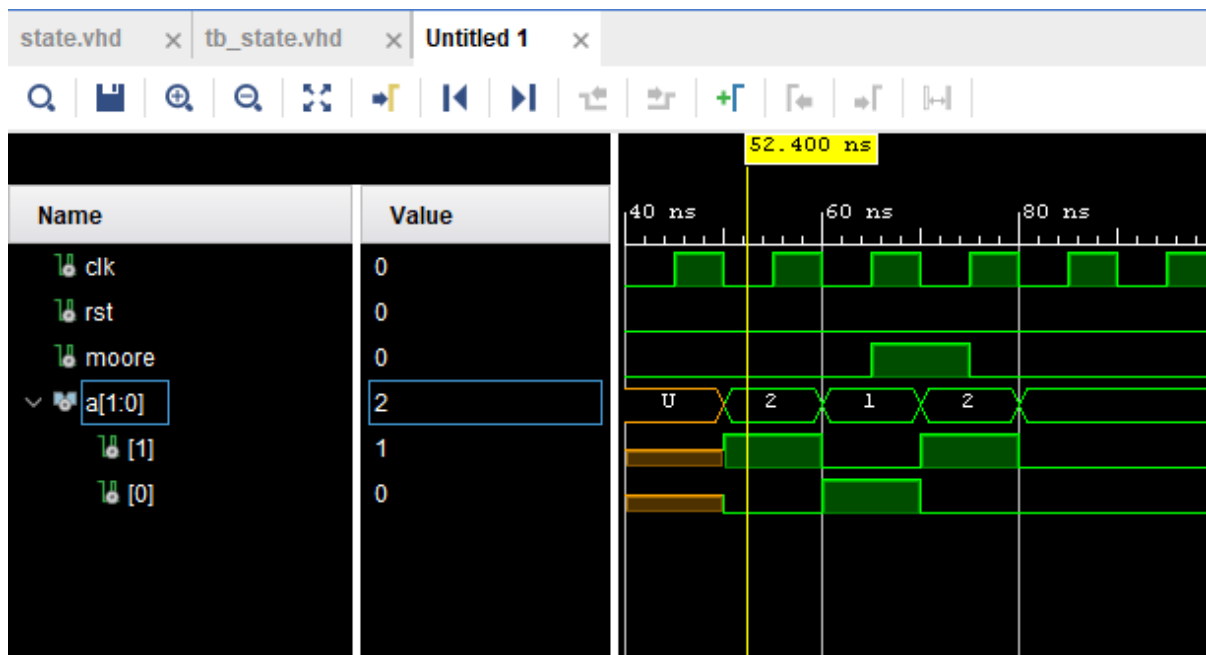

Elaborated Schematic:

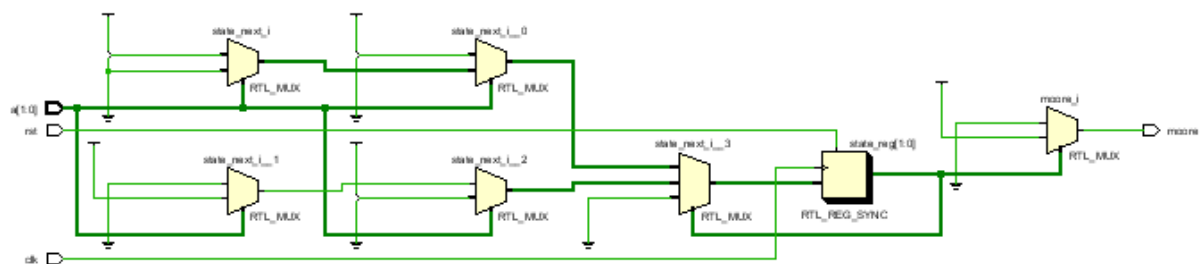

Implementation Schematic:

 

Utilization Report:

Name	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Logic (53200)	Block RAM Tile (140)	Bonded IPADs (2)	BUFIO (16)
state	2	2	1	2	2	5	1

Problem 2

Design a circuit that outputs a given sequence of bits.

- Send LSB first.
- Sequence should start with 4 1s and ends with 4 0s.
- Make the sequence 8-bits long.
- The default output should stay at 0.
- Example: For a sequence of 10111011, the output should look like 1111110111010000.
- When the transmission ends, generate a transmission done signal.
- The data is passed into the circuit using an 8-bit port.

An example entity is given below:

```
entity sequencer is
generic (
    D : integer := 8 -- data bits
);
port (
    clk, rst : in std_logic;
    i_start : in std_logic; -- start transmission
    i_data : in std_logic_vector(D-1 downto 0); -- send this data
    o_tx : out std_logic; -- transmission out
    o_tx_done : out std_logic -- transmission done
);
end sequencer;
```

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity sequencer is
generic (
    D : integer := 8 -- data bits
);
port (
    clk, rst : in std_logic;
    i_start : in std_logic; -- start transmission
    i_data : in std_logic_vector(D-1 downto 0); -- send this data
    o_data : out std_logic_vector(D+7 downto 0) := "0000000000001111";
    o_tx : out std_logic; -- transmission out
    o_tx_done : out std_logic -- transmission done
);
end sequencer;

architecture Behavioral of sequencer is
```

```

signal t_done : std_logic;
signal i_data_reverse : std_logic_vector(D-1 downto 0);
type state_type is (s0, s1, s2);
signal state, state_next : state_type := s0;

begin

process(clk) is
begin
    if rising_edge(clk) then
        if rst = '1' then
            state <= s0;
        else
            state <= state_next;
        end if;
    end if;
end process;

process(state, i_data) is
begin
    case state is
        when s0 =>
            if i_start <= '1' then
                state_next <= s1;
            end if;
        when s1 =>
            i_data_reverse(7) <= i_data(0);
            i_data_reverse(6) <= i_data(1);
            i_data_reverse(5) <= i_data(2);
            i_data_reverse(4) <= i_data(3);
            i_data_reverse(3) <= i_data(4);
            i_data_reverse(2) <= i_data(5);
            i_data_reverse(1) <= i_data(6);
            i_data_reverse(0) <= i_data(7);

            o_data(11 downto 4) <= i_data_reverse;
            state_next <= s2;
        when s2 =>

```



```

        state_next <= s0;

    end case;
end process;

process(state) is
begin
    case state is
        when s0 | s1 =>
            o_tx_done <= '0';
        when s2 =>
            o_tx_done <= '1';
        end case;
    end process;

end Behavioral;

```

Testbench Code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_sequencer is
end tb_sequencer;

architecture Behavioral of tb_sequencer is
    component sequencer is
    generic (
        D : integer := 8 -- data bits
    );
    port (
        clk, rst : in std_logic;
        i_start : in std_logic; -- start transmission
        i_data : in std_logic_vector(D-1 downto 0); -- send this data
        o_data : out std_logic_vector(D+7 downto 0) := "000000000001111";
        o_tx : out std_logic; -- transmission out
        o_tx_done : out std_logic -- transmission done
    );
end component;

```

```

signal clk,rst,i_start,o_tx_done : std_logic;
signal i_data : std_logic_vector(7 downto 0);
signal o_data : std_logic_vector(15 downto 0);

begin

h0: sequencer port map(
clk=>clk, rst=>rst, i_start=>i_start, o_tx_done=>o_tx_done, i_data=>i_data, o_data=>o_data);

clock_process :process
begin
rst <='0';
clk <='0';
wait for 5 ns;
clk <= '1';
wait for 5 ns;
end process;



process
begin
wait for 50 ns;
i_start <= '1';
wait for 10 ns;
i_data <= "01100000";
wait for 10 ns;
i_start <= '0';
wait for 10 ns;
i_data <= "01100000";
wait for 10 ns;
i_start <= '1';
wait for 10 ns;
i_data <= "01110100";
wait;

end process;

end Behavioral;


```

Simulation:

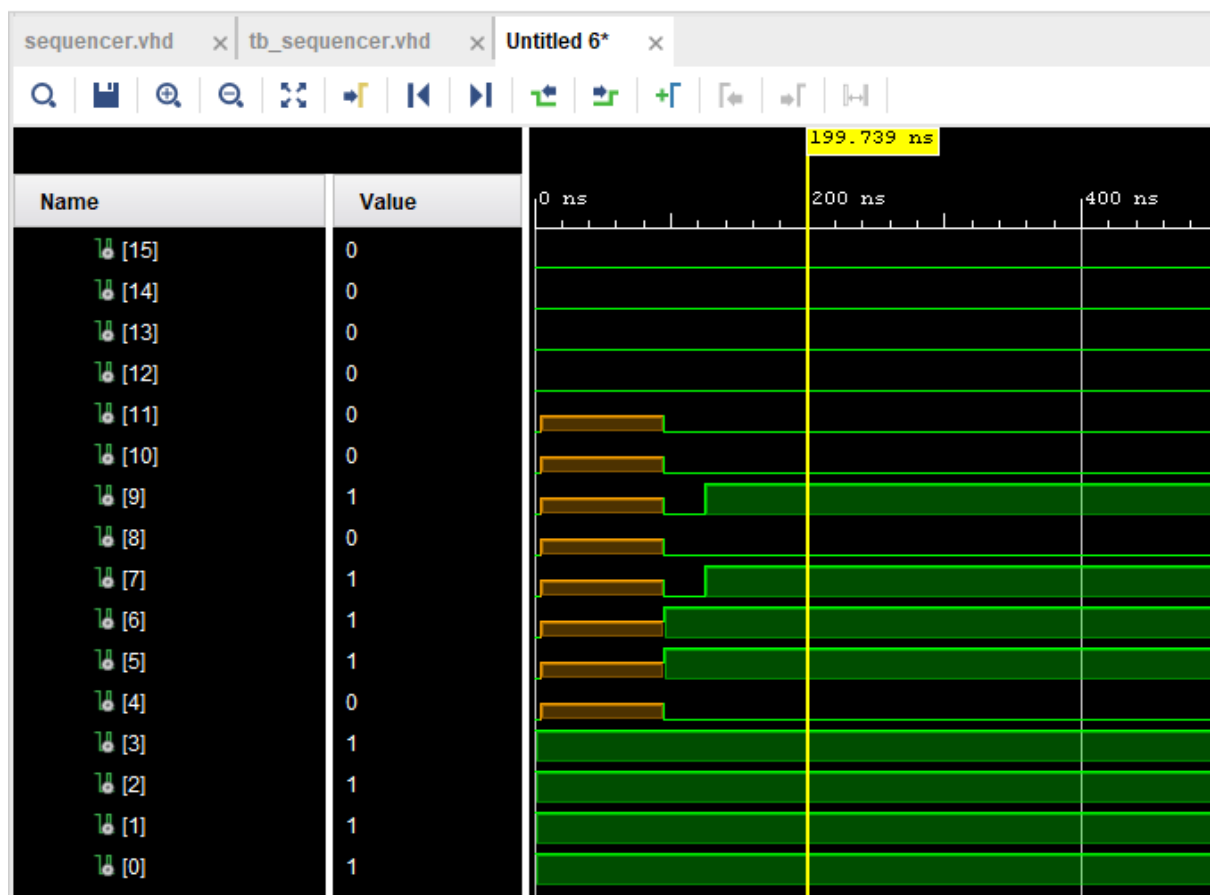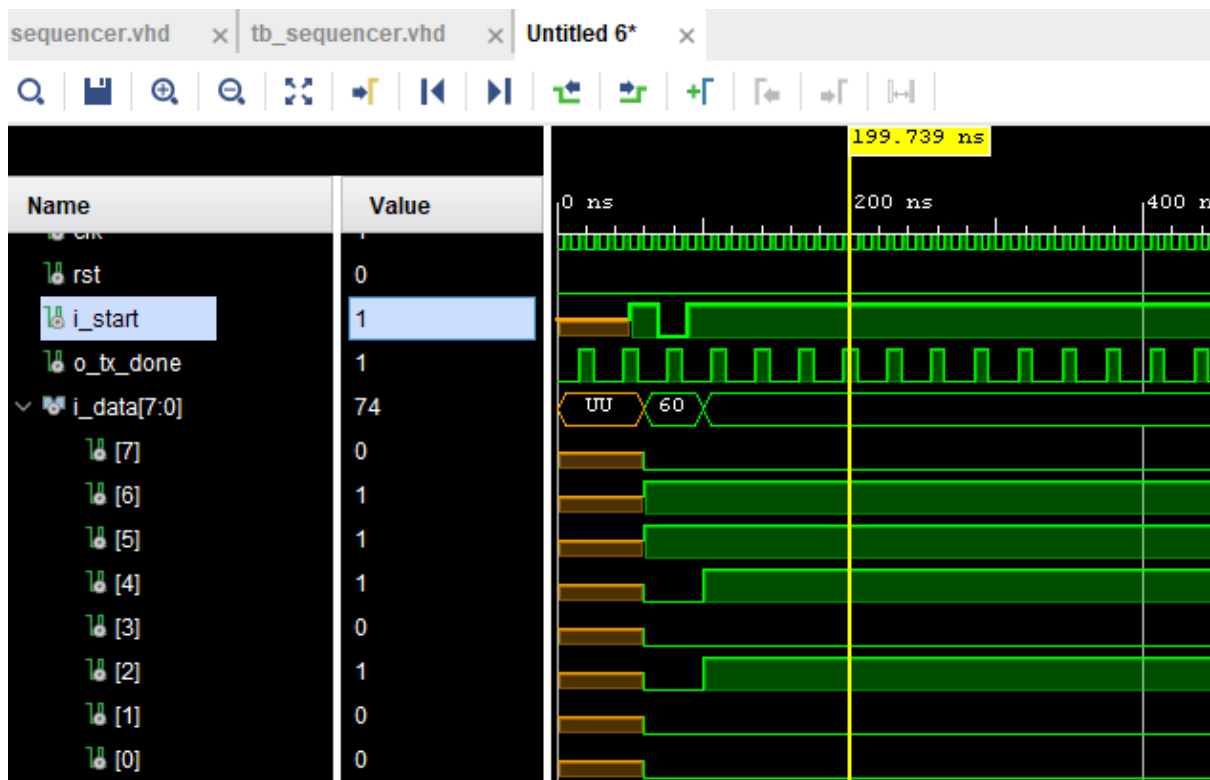


Input: 01110100 , Output: 000001011101111

Elaborated Schematic:

 

Implementation Schematic:

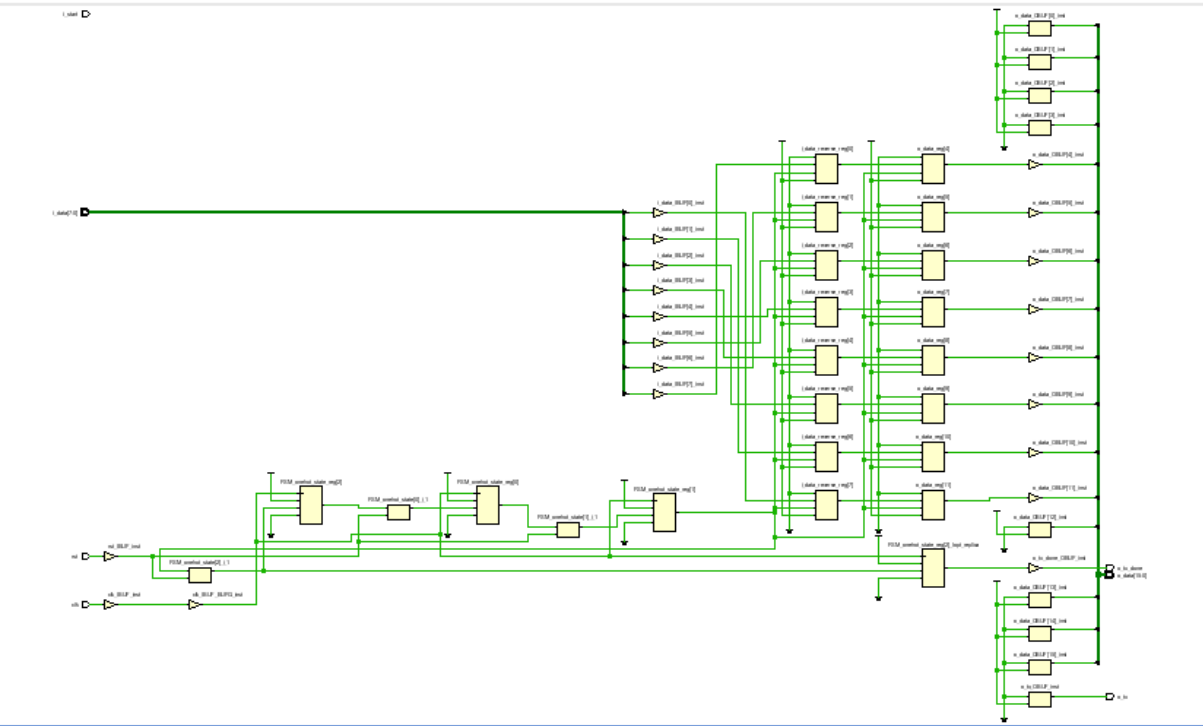

Utilization Report:

Name	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Logic (53200)	Block RAM Tile (140)	Bonded IPADs (2)	BUFIO (16)
sequencer	2	20	5	2	20	28	1

Problem 3

Based on the circuit that you designed in *sequencer* problem, implement a multi-cycle clone. Meaning that, each bit that you send should stay for a given number of clock cycles denoted below using the *M* generic. Use the timer circuit that you built before for this purpose.

```
entity serializer is
generic (
    D : integer := 8; -- data bits
    M : integer := 10 -- how many cycles the signals should be transmitted
);
port (
    clk, rst : in std_logic;
    i_start : in std_logic;
    i_data : in std_logic_vector(D-1 downto 0);
    o_tx : out std_logic;
    o_tx_done : out std_logic
);
end serializer;
```

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity sequencer is
generic (
    D : integer := 8; -- data bits
    M : integer := 10
);
port (
    clk, rst : in std_logic;
    i_start : in std_logic := '0'; -- start transmission
    i_data : in std_logic_vector(D-1 downto 0); -- send this data
    o_data : out std_logic_vector(D+7 downto 0) := "0000000000000000";
    o_tx : out std_logic; -- transmission out
    o_tx_done : out std_logic -- transmission done
);
end sequencer;

architecture Behavioral of sequencer is
    signal t_done : std_logic;
    signal i_data_reverse : std_logic_vector(D-1 downto 0);
    type state_type is (s0, s1, s2);
    signal state, state_next : state_type := s0;
```

```
signal cnt, cnt_next : integer range 0 to M := 0;
signal trgt, trgt_next : integer range 0 to M := 0;
```

```
begin
```

```
process(clk) is
```

```
begin
```

```
    if rising_edge(clk) then
```

```
        if rst = '1' then
```

```
            state <= s0;
```

```
        else
```

```
            state <= state_next;
```

```
            cnt <= cnt_next;
```

```
            trgt <= trgt_next;
```

```
        end if;
```

```
    end if;
```

```
end process;
```

```
process(state, i_data,cnt,trgt) is
```

```
begin
```

```
state_next <= state;
```

```
cnt_next <= cnt;
```

```
trgt_next <= trgt;
```

```
case state is
```

```
when s0 =>
```

```
    if i_start <= '1' then
```

```
        cnt_next <= 0;
```

```
        state_next <= s1;
```

```
    else
```

```
        state_next <= s0;
```

```
    end if;
```

```
when s1 =>
```

```
    i_data_reverse(7) <= i_data(0);
```

```
    i_data_reverse(6) <= i_data(1);
```

```
    i_data_reverse(5) <= i_data(2);
```

```
    i_data_reverse(4) <= i_data(3);
```

```
    i_data_reverse(3) <= i_data(4);
```

```
    i_data_reverse(2) <= i_data(5);
```

```
    i_data_reverse(1) <= i_data(6);
```

```

        i_data_reverse(0) <= i_data(7);
        o_data(11 downto 4) <= i_data_reverse;
        o_data(15 downto 12) <= "0000";
        o_data(3 downto 0) <= "1111";
        if cnt = M-2 then
            state_next <= s2;
        else
            cnt_next <= cnt +1;
        end if;
    when s2 =>
        state_next <= s0;

end case;
end process;

process(state) is
begin
    case state is
        when s0 =>
            o_tx_done <= '0';
            o_tx <= '0';
        when s1 =>
            o_tx_done <= '0';
            o_tx <= '1';
        when s2 =>
            o_tx_done <= '1';
            o_tx <= '1';
        end case;
    end process;

end Behavioral;

```

Testbench Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_sequencer is
end tb_sequencer;

architecture Behavioral of tb_sequencer is
  component sequencer is
    generic (
      D : integer := 8 -- data bits
    );
    port (
      clk, rst : in std_logic;
      i_start : in std_logic; -- start transmission
      i_data : in std_logic_vector(D-1 downto 0); -- send this data
      o_data : out std_logic_vector(D+7 downto 0) := "0000000000001111";
      o_tx : out std_logic; -- transmission out
      o_tx_done : out std_logic -- transmission done
    );
  end component;

  signal clk,rst,i_start,o_tx_done,o_tx : std_logic;
  signal i_data : std_logic_vector(7 downto 0);
  signal o_data : std_logic_vector(15 downto 0);

begin

  h0: sequencer port map(
    o_tx => o_tx, clk=>clk, rst=>rst, i_start=>i_start, o_tx_done=>o_tx_done, i_data=>i_data,
    o_data=>o_data);

  clock_process :process
  begin
    rst <='0';
    clk <='0';
    wait for 5 ns;
    clk <= '1';
    wait for 5 ns;
  end process;

  process
```




```

begin
i_start <= '1';
i_data <= "01100000";
wait;


end process;
end Behavioral;

```


Simulation:

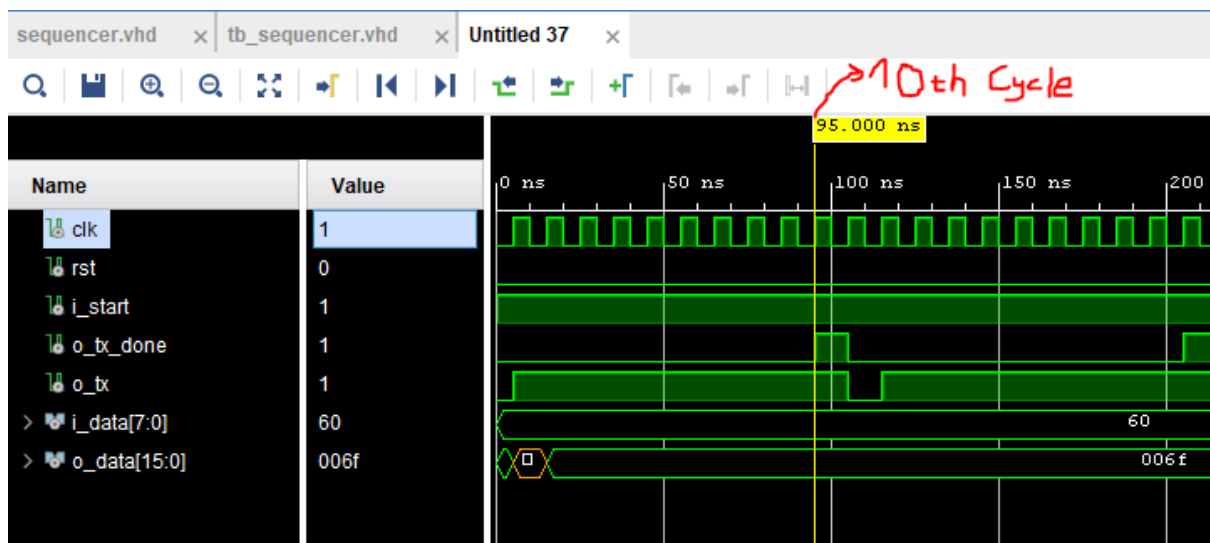

Elaborated Schematic:

 

Implementation Schematic:

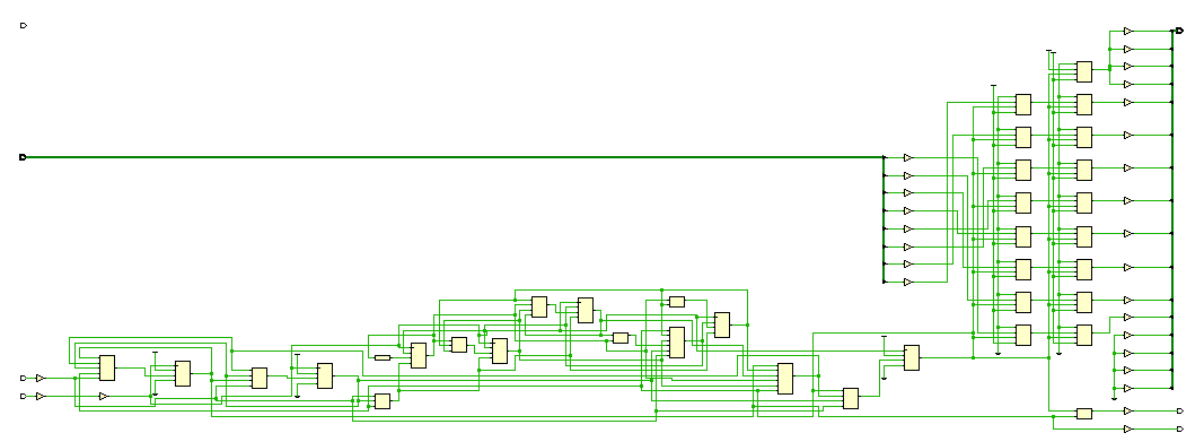

Report Utilization

Name	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Logic (53200)	Block RAM Tile (140)	Bonded IPADs (2)	BUFIO (16)
N sequencer	8	24	10	8	24	28	1