

ELEC 457

Assignment-4

Sait Berk VARIMLI

141024054

I prepare this assignment in 14 hour.

Problem 1

Design and simulate an **8-bit adder** using `numeric_std` package supplied `+` operator. Compare utilization and timing characteristics with the previous two adders that you designed in assignment 3.

Design Code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity adder8b is
    port
    (
        a, b : in unsigned(7 downto 0);
        sum   : out unsigned(7 downto 0);
        carry_out : out std_logic
    );
end entity adder8b;

architecture Behavioral of adder8b is
    signal temp : unsigned(8 downto 0);
begin
    temp <= ("0" & a) + b;
    sum   <= temp(7 downto 0);
    carry_out <= temp(8);
end architecture Behavioral;
```

Testbench code:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
entity tb_adder8b is
```

```
END tb_adder8b;
```

```
architecture arch12 of tb_adder8b is
```

```
component adder8b is
```

```
port (a, b : in unsigned(7 downto 0);
```

```
      carry_out:out std_logic;
```

```
      sum:out unsigned(7 downto 0));
```

```
end component;
```

```
signal a,b,sum:unsigned(7 downto 0);
```

```
signal carry_out :std_logic;
```

```
begin
```

```
    a0 : adder8b port map(
```

```
    a => a , b => b , sum => sum, carry_out => carry_out );
```

```
    process
```

```
    begin
```

```
        wait for 100 ns;
```

```
        a <= "00000001";
```

```
        b <= "00000001";
```

```
        wait for 30 ns;
```

```
        a <= "00001001";
```

```
        b <= "00000101";
```

```
        wait for 30 ns;
```

```
        a <= "00010001";
```

```
        b <= "00001001";
```

```

wait for 30 ns;

a <= "01001101";

b <= "00110101";

wait for 30 ns;

a <= "11011101";

b <= "11110001";

wait for 30 ns;

a <= "11100111";

b <= "01011101";

wait for 30 ns;

a <= "11111111";

b <= "11111111";

wait;

end process;


end arch12;

```

Time Simulation Differences;


With new adder;

Lag is 5.66 ns

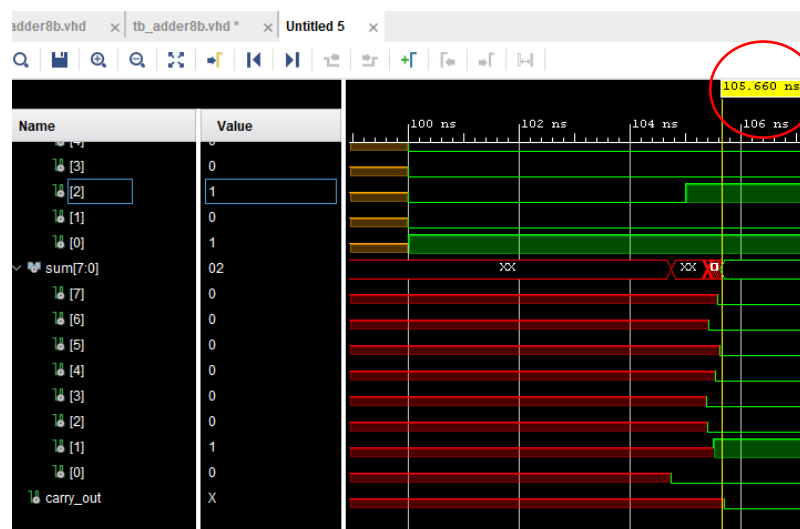

With previous adder;

Lag is 9.06ns

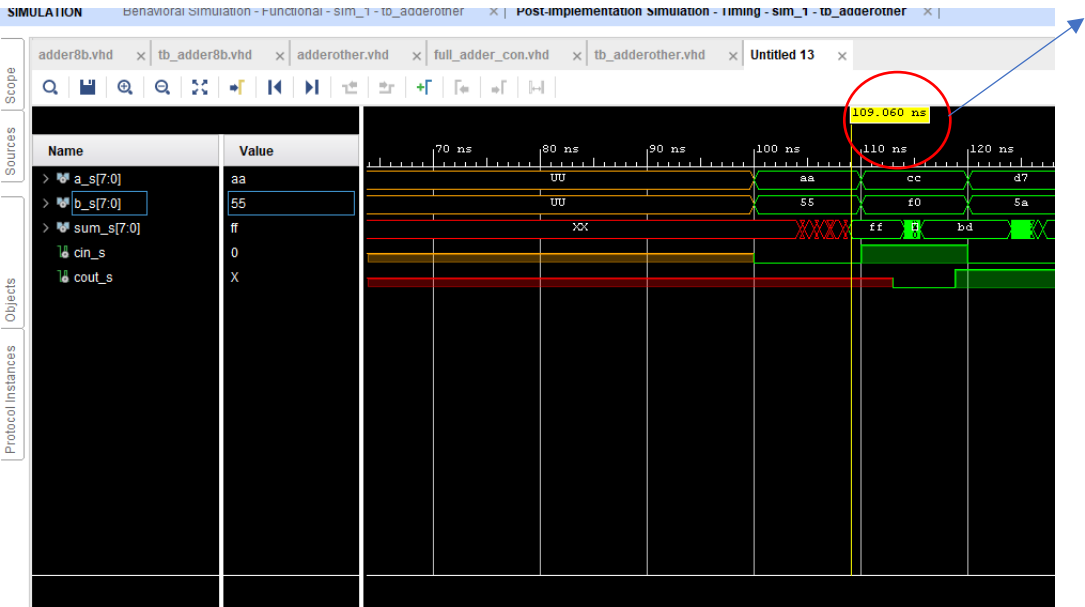

Utilization Differences;

With new adder;

Name	Slice LUTs (53200)	Slice (13300)	LUT as Logic (53200)	Bonded IPADs (2)
adder8b	8	3	8	25

With old adder;

Name	Slice LUTs (53200)	Slice (13300)	LUT as Logic (53200)	Bonded IPADs (2)
adderother	8	3	8	26

Problem 2

Design and simulate a **32-bit barrel shifter**. Shift the 32-bit input by the selected amount with the `sel` input, and selected orientation with the `ori` input.

Design Code:

```
library ieee;

use ieee.std_logic_1164.all;

entity barrels is

port (clk,reset,ori :in std_logic;

sel:in std_logic_vector (31 downto 0);

output:out std_logic_vector (31 downto 0));

end barrels;

architecture Barrel of barrels is

begin

process (reset,clk,sel)

variable d: std_logic_vector (31 downto 0);

begin

if (reset = '0') then

d:=(others => '0');

elsif (clk'event and clk = '1') then

if (ori ='1') then

d:=sel;

else

d:= d(0) & d(31 downto 1) ;

end if;

end if;

output<= d;
```

```
end process;
```

```
end barrel;
```

Testbench Code:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity tb_Barrels is
```

```
end tb_Barrels;
```

```
architecture tb_Barrel of tb_Barrels is
```

```
component Barrels
```

```
port (clk,reset,ori :in std_logic;
```

```
sel:in std_logic_vector (31 downto 0);
```

```
output:out std_logic_vector (31 downto 0));
```

```
end component;
```

```
signal clk,res,ori : std_logic;
```

```
signal d_in,d_out : std_logic_vector (31 downto 0);
```

```
begin
```

```
br: Barrels port map (clk,res,ori,d_in,d_out);
```

```
process
```

```
begin
```

```
res <= '1'; ori <= '1';
```

```
wait for 5 ns;
```

```
ori <= '1';
```

```
clk<='0';
```

```
d_in<="11111101111111011100010111111101";
```

```
wait for 5 ns;
```

```

clk<='1';

d_in<="000011011111111011100010111000101";

wait for 5 ns;

res <= '1';

d_in <= "00000101110001011100010111000101";

ori <= '1';

wait for 5 ns;

ori <= '0';


wait;

end process;


end tb_Barrel;

```


Simulation:

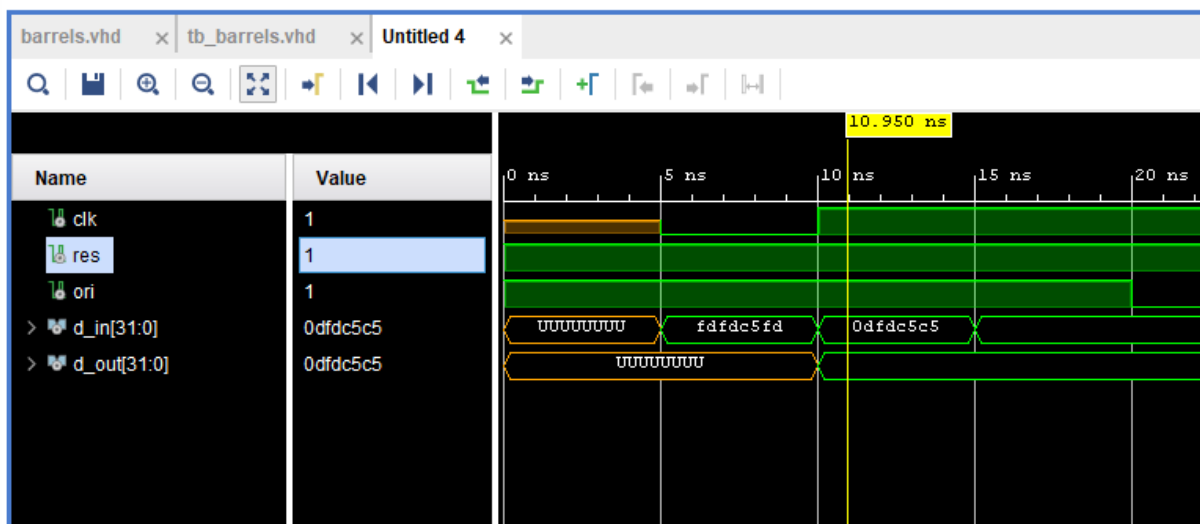

Elaborated Schematic:

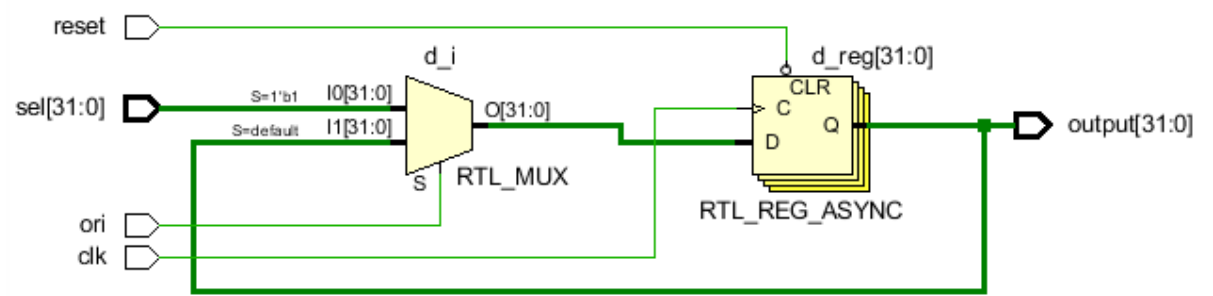

Implementation Schematic:

 

Utizilation Report:

Name	Slice LUTs (53200)	Slice Registers (106400)	Slice (13300)	LUT as Logic (53200)	Block RAM Tile (140)	Bonded IPADs (2)	BUFIO (16)
N barrels	17	64	13	17	64	67	1

Problem 3

Design and simulate a **parity generator** for 8-bit values. Check out the timing and figure out how long it takes. Auto test your results with a *smarter* simulation.

Code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity parityg is
    Port (
        input: in std_logic_vector(7 downto 0);
        odd : out std_logic);
end parityg;

architecture Behavioral of parityg is
    signal s : std_logic_vector(6 downto 0);
begin
    s(0) <= input(0) xor input(1);
    s(1) <= input(2) xor input(3);
    s(2) <= input(4) xor input(5);
    s(3) <= input(6) xor input(7);
    s(4) <= s(0) xor s(1);
    s(5) <= s(2) xor s(3);
    odd <= s(4) xor s(5);

end Behavioral;
```

Testbench Code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity tb_parityg is
end tb_parityg;

architecture Behavioral of tb_parityg is
    component parityg is
    Port (
        input: in std_logic_vector(7 downto 0);
        odd: out std_logic );
    end component;

    signal input : std_logic_vector(7 downto 0);
    signal odd : std_logic;

    begin

        s0 : parityg port map(
            input => input, odd => odd
        );

        process

        begin

            wait for 50 ns;

            input <= "00000000";

            wait for 10 ns;


            input <= "00000001";

            wait for 10 ns;


            input <= "00001100";
```

```
wait for 10 ns;  
  
input <= "00100000";  
  
wait;  
  
end process;  
  
end Behavioral;
```


Simulation:

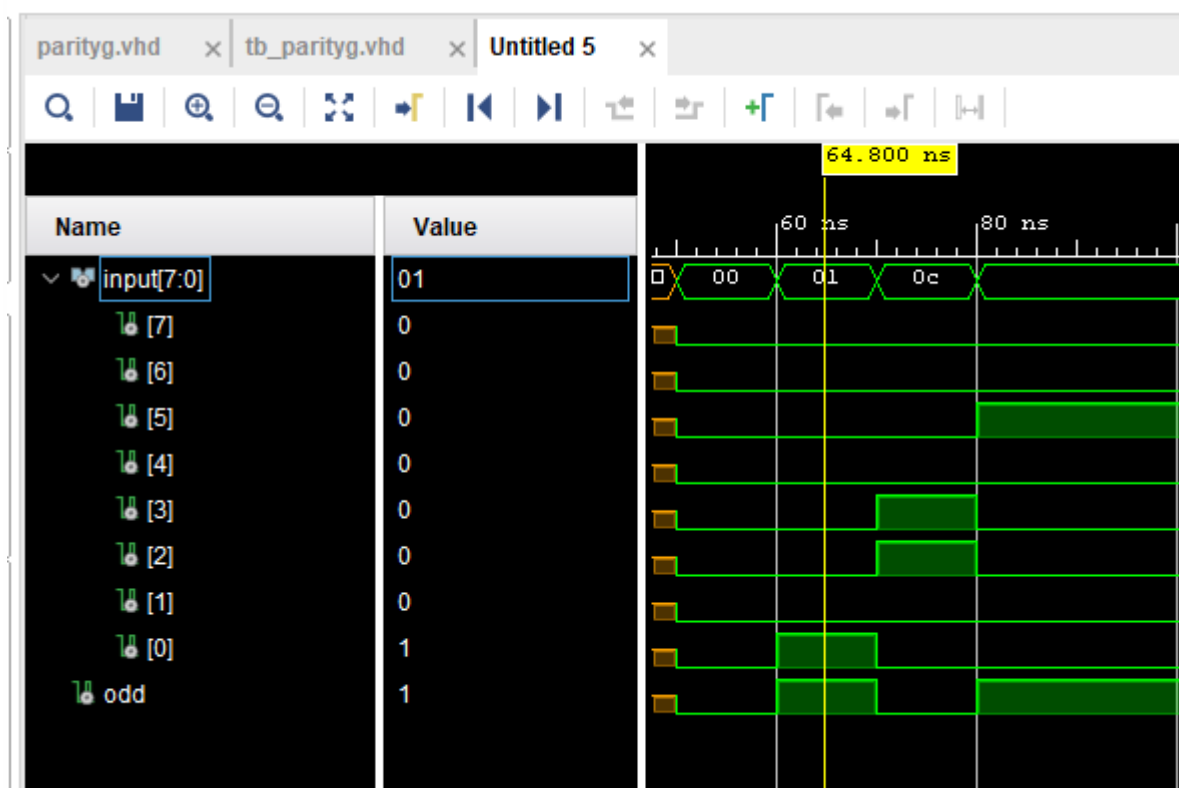

Eloborated Design:

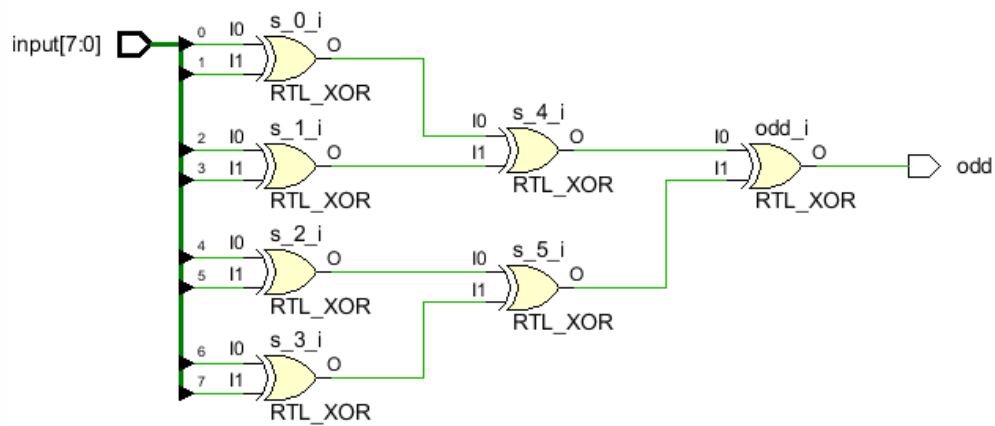


Implementation Design:

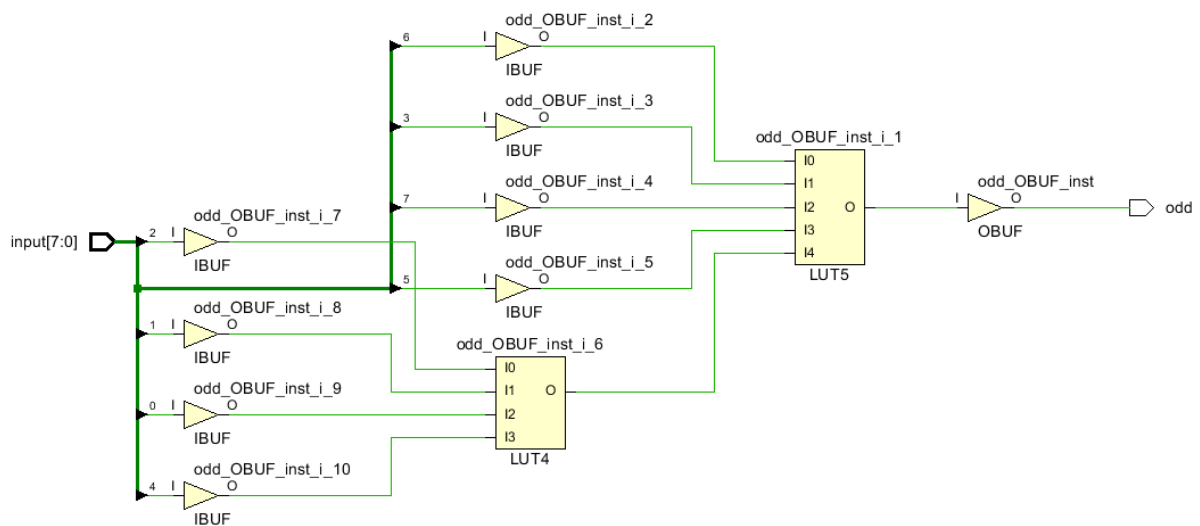

Utizilation Report:

Name ^ 1	Slice LUTs (53200)	Slice (13300)	LUT as Logic (53200)	Bonded IPADs (2)
N parityg	2	2	2	9

Timing Simulation:

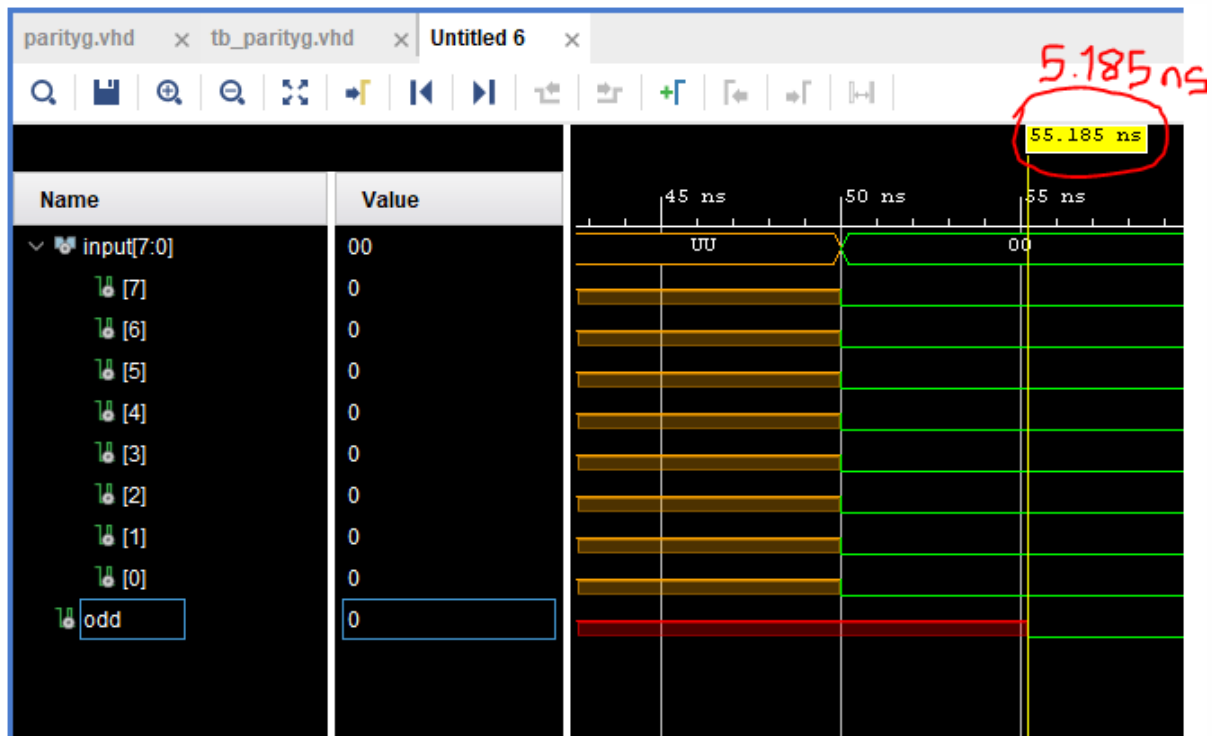

Problem 4

Design and simulate an 32-to-5 **priority encoder**. You can design and utilize smaller encoders (structural design). Auto test your results with a *smarter* simulation.

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity priority32t5 is
    Port (
        e : in std_logic;
        input : in std_logic_vector(31 downto 0);
        output : out std_logic_vector(4 downto 0)
    );
end priority32t5;

architecture Behavioral of priority32t5 is

begin
    process (e, input) begin
        output <= "00000";
        if (e = '1') then
            if (input(31 downto 27) = "00001") then
                output <= "00001";
            elsif (input(31 downto 27) = "00010") then
                output <= "00010";
            elsif (input(31 downto 27) = "00011") then
                output <= "00011";
            elsif (input(31 downto 27) = "00100") then
                output <= "00100";
            elsif (input(31 downto 27) = "00101") then
                output <= "00101";
            elsif (input(31 downto 27) = "10010") then
```

```

        output <= "10010";
    elsif (input(31 downto 27) = "10100") then
        output <= "10100";
    elsif (input(31 downto 27) = "11000") then
        output <= "11000";
    elsif (input(31 downto 27) = "11001") then
        output <= "11001";
    elsif (input(31 downto 27) = "11010") then
        output <= "11010";
    elsif (input(31 downto 27) = "11100") then
        output <= "11100";
    elsif (input(31 downto 27) = "11110") then
        output <= "11110";
    elsif (input(31 downto 27) = "11111") then
        output <= "11111";
    else
        output <= "00000";
    end if;
end if;
end process;
end Behavioral;

```

Testbench:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_priority32t5 is
end tb_priority32t5;

architecture Behavioral of tb_priority32t5 is
    component priority32t5 is
    Port (
        e : in std_logic;

```



```

    input : in std_logic_vector(31 downto 0);
    output : out std_logic_vector(4 downto 0)
);
end component;

signal e : std_logic;
signal input : std_logic_vector(31 downto 0);
signal output : std_logic_vector(4 downto 0);
begin
    s0 : priority32t5 port map(
    e => e, input => input, output => output
    );
    process
    begin
        wait for 50 ns;
        e <= '1';
        input <= "00001000000000000000000000000000";
        wait for 5 ns;
        e <= '1';
        input <= "11100000000000000000000000000000";
        wait for 5 ns;
        e <= '1';
        input <= "11110000010000000000000000000000";
        wait for 5 ns;
        e <= '1';
        input <= "11011000001000000000000000000000";
        wait for 5 ns;
        e <= '1';
        input <= "01010000001000000000000000000000";
        wait for 5 ns;
        e <= '1';
        input <= "00000000001000000000000000000000";
        wait for 5 ns;

```


```

end process;

end Behavioral;

```


Simulation:

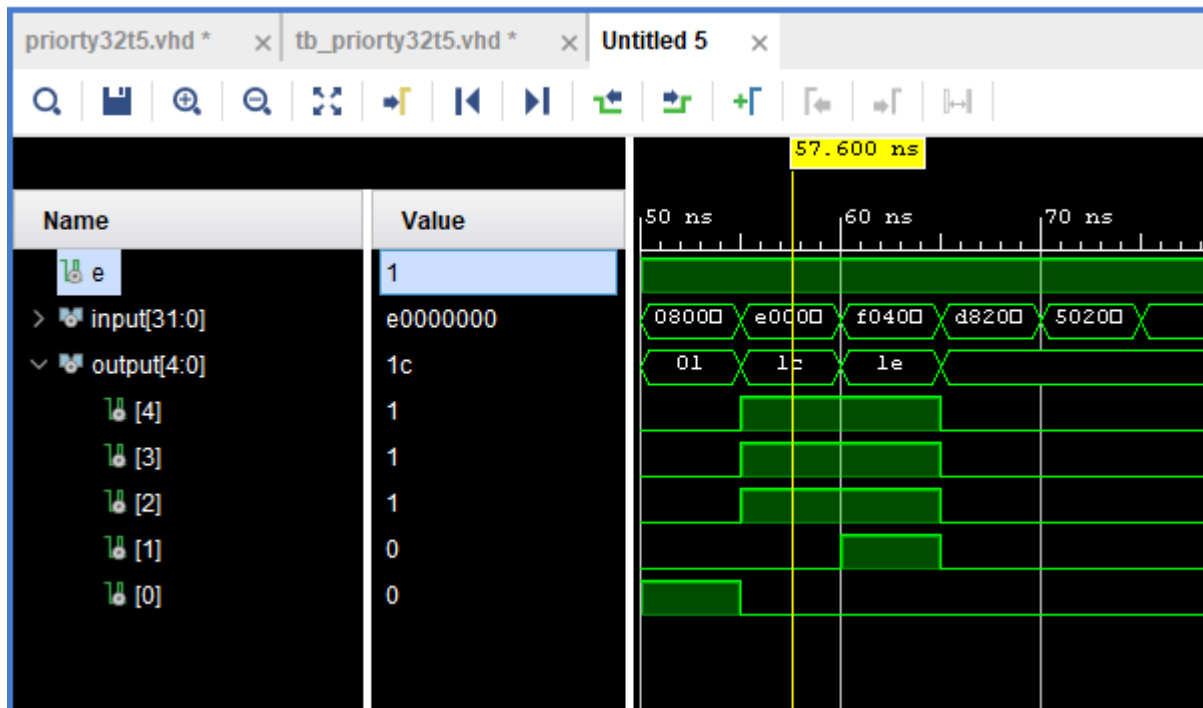

Elaborated Schematic:



Implementation Schematic:

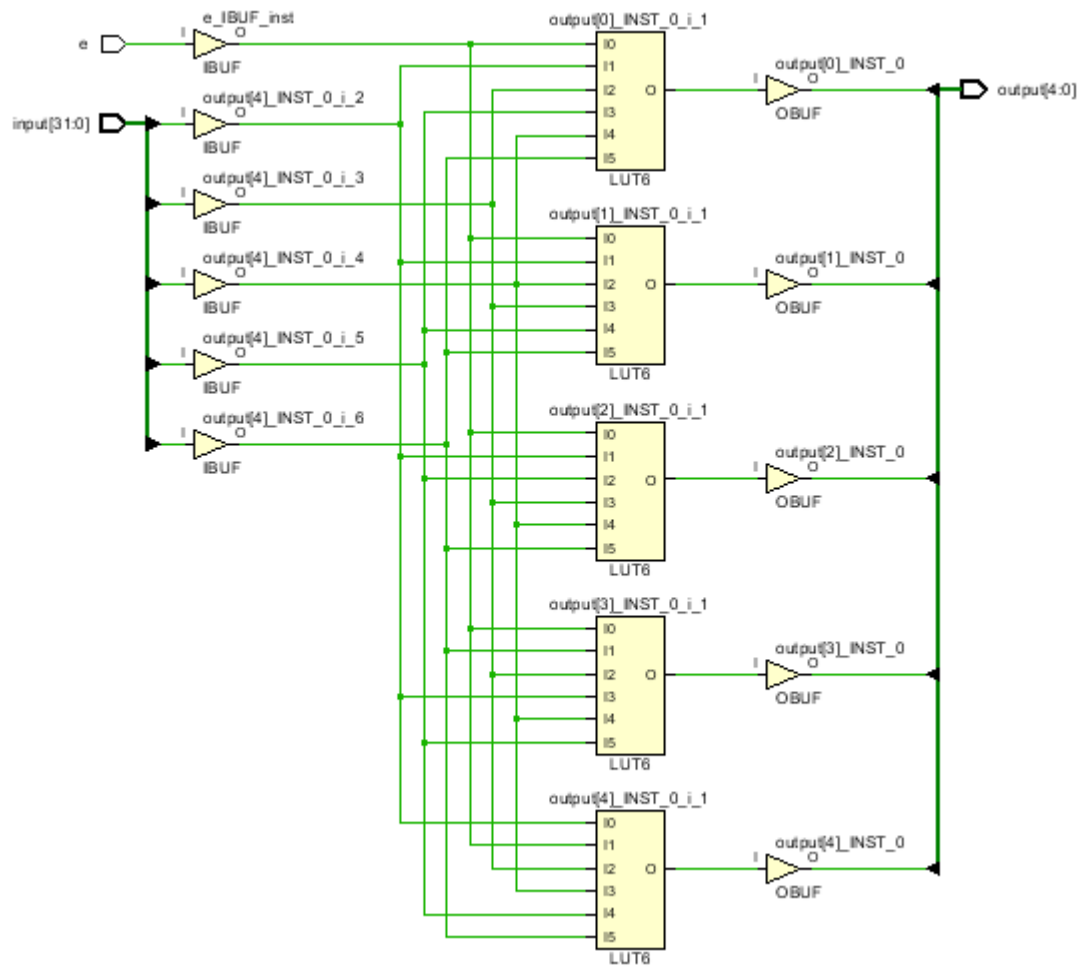

Utilization Report:

Name	Slice LUTs (53200)	Slice (13300)	LUT as Logic (53200)	Bonded IPADs (2)
N priority32t5	5	2	5	11

Previous Homework

Problem 5

Design and simulate an **RGB to YUV converter**. Your circuit should have a 24-bit input consisting of 8-bit red, 8-bit green and 8-bit blue values in that order. You should have 24-bit YUV output. You can use the following formulation;

For simulation, just pick 16 random colors with 5 of them being black, white, just blue, just red and just green.

For this problem, firstly i understood that i had to do with fixed_pkg library but i couldn't use this library. When i tried to add this library i got some errors and i couldn't setup it. After that without fixed_pkg library, my method for float number was first multiple those numbers(0.299, etc.) with 2^{17} and make them as integer, after calculation with equation, divide every result with 2^{17} . I wrote some code but i couldn't divide them.

My design code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity rgbtoyuv is

Port (

    rxy : in integer:=39191; --0.299 * 2^17 etc.

    gyy : in integer:=76939;

    bzy : in integer:=14942;

    rxu : in integer:=19268;

    gyu : in integer:=37880;

    bzu : in integer:=57148;
```

```

rxv : in integer:=80610;
gyv : in integer:=67502;
bzv : in integer:=13107;
rgb : in unsigned(23 downto 0):="000010001100011010011001";--example
y,u,v : out std_logic_vector(7 downto 0)
);
end rgbtoyuv;

architecture Behavioral of rgbtoyuv is
begin
process
variable intr,intg,intb, inty,intu,intv : integer;

variable cons : std_logic_vector(23 downto
0):="000000100000000000000000"; --it is 2^17 in binary

begin

intr := to_integer(rgb(23 downto 16));
intg := to_integer(rgb(15 downto 8));
intb := to_integer(rgb(7 downto 0));

inty := ((rxy * intr) + (gyy * intg) + (bzy * intb)) ;
intu := ((-rxu * intr) + (-gyu * intg) + (bzu * intb));
intv := ((rxv * intr) + (-gyv * intg) + (-bzv * intb));

y <= std_logic_vector(to_signed(inty,8));
u <= std_logic_vector(to_signed(intu,8));
v <= std_logic_vector(to_signed(intv,8));

end process;

end Behavioral;

```

Problem 6

Design and simulate a **hamming distance** finder. Your circuit should have a generic for input bit with, two n-bit inputs to calculate the hamming distance and an 8-bit output to send the result. Find a suitable algorithm. Test 16 random selected pairs for the simulation.

Design Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;
entity hamming is
generic ( N : integer := 32);
port(
i_a, i_b : in std_logic_vector(N-1 downto 0);
o_dist : out std_logic_vector(7 downto 0));
end hamming;
architecture Behavioral of hamming is
signal difference : std_logic_vector(N-1 downto 0) := (others => '0');
function sum ( s : std_logic_vector ) return natural is
    variable sum : integer range 0 to s'length := 0;
begin
for x in s'range loop
if s(x) = '1' then
sum := sum+1;
else
sum := sum;
end if;
end loop;
return sum;
end function;
begin
```

```

difference <= i_a xor i_b ;
o_dist <= std_logic_vector(to_unsigned(sum(difference),8));
end Behavioral;

```

Testbench Code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_hamming is
end tb_hamming;

architecture Behavioral of tb_hamming is
    component hamming is
    generic ( N : integer := 32);
    port(
        i_a, i_b : in std_logic_vector(N-1 downto 0);
        o_dist : out std_logic_vector(7 downto 0));
    end component;

    signal i_a,i_b : std_logic_vector(31 downto 0);
    signal o_dist  : std_logic_vector(7 downto 0);

begin

h0: hamming port map(
    i_a => i_a, i_b=>i_b, o_dist=>o_dist);

process
begin
    wait for 50 ns;

    i_a <= "00000000000000000000000000000000110";
    i_b <= "00000000000000000000000000000000000";
    wait for 10 ns;



    i_a <= "0000000000000000000000000000000010";
    i_b <= "00000000000000000000000000000000000";
    wait for 10 ns;

    i_a <= "000000010000010000000000000000110";
    i_b <= "000000000000000001000001000000000";
    wait for 10 ns;
end process


```

[illegible]


Simulation:

  

End

 

Implementation Schematic:

 

Utizilation Report:

Name ¹	Slice LUTs (53200)	Slice (13300)	LUT as Logic (53200)	Bonded IPADs (2)
N hamming	44	12	44	72